

# Improving FM Combiner/Filter Efficiency and Size Using Non-Conventional Coupling

Presented By: Daniel S Fallon  
Sr. RF Engineer

The logo for Dielectric, featuring the word "Dielectric" in a blue serif font with a red swoosh above the letter 'i'.

Dielectric®

**Trusted for Decades. Ready for Tomorrow.**




## AGENDA

- FM Combining Basics
  - Transmitter Intermodulation
  - Constant impedance filter(CIF) and Brach Combiners
- Efficiency for Chebychev and Cross-Coupled Filters
- Source / Load Coupling
- Relative advantages and dis-advantages of CIF and Manifold Combining


# Intermodulation Generation – Co-site Interference

Antenna

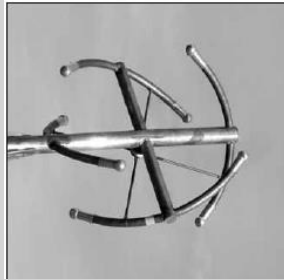


- $2f_1 - f_2$  is in FM or Air Nav Band
- $P_{IM} \sim P_{f_1} + P_{f_2} - TAL$
- - 80 dB is IM power spec

Transmitter

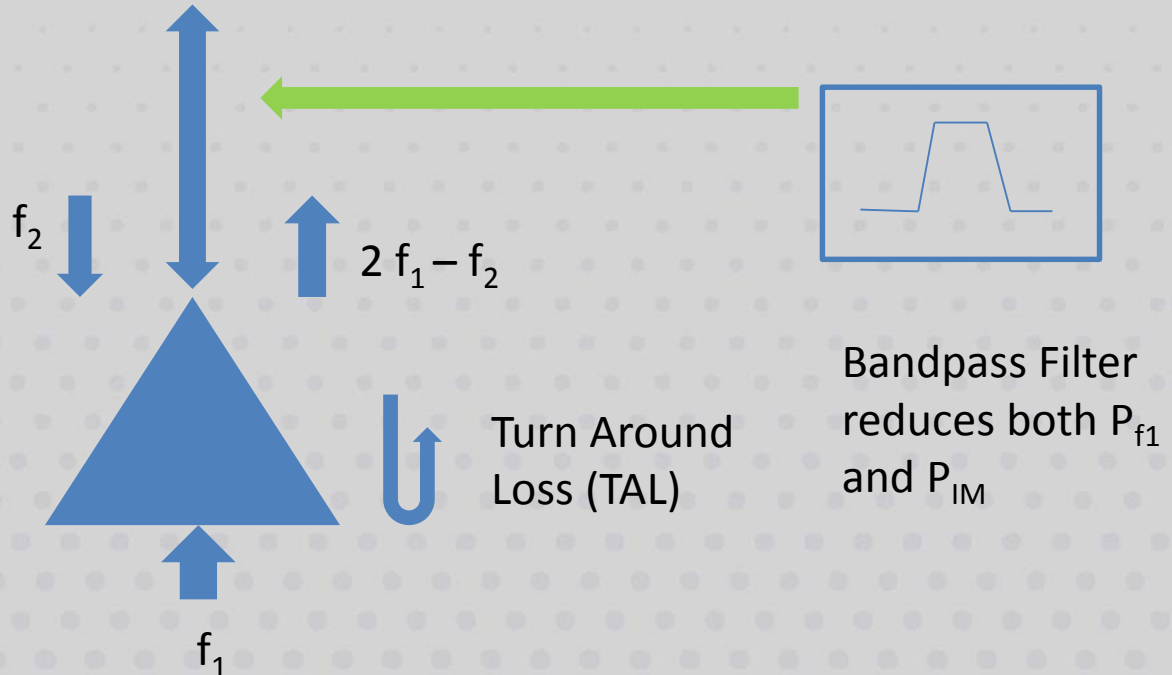


# Intermodulation Generation – Channel Combining

Antenna

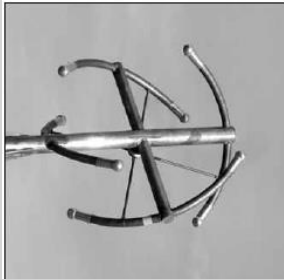

Coaxial Tee

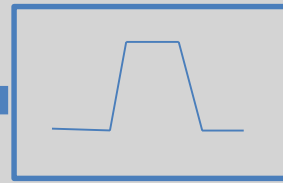


$f_2$

$2f_2 - f_1$

TAL<sub>2</sub>

Bandpass Filter

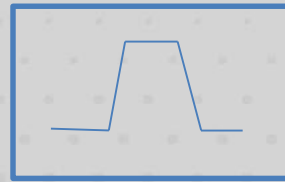

$2f_1 - f_2$

Branch Topology  
a.k.a. Star Point  
or Manifold

Transmitter




Turn Around Loss (TAL)

$f_1$


# Intermodulation Generation – Channel Combining

Antenna

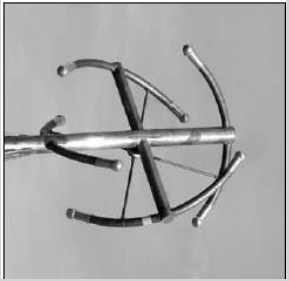


Constant Impedance Filter (CIF) Topology  
a.k.a. Balanced or Directional Filter

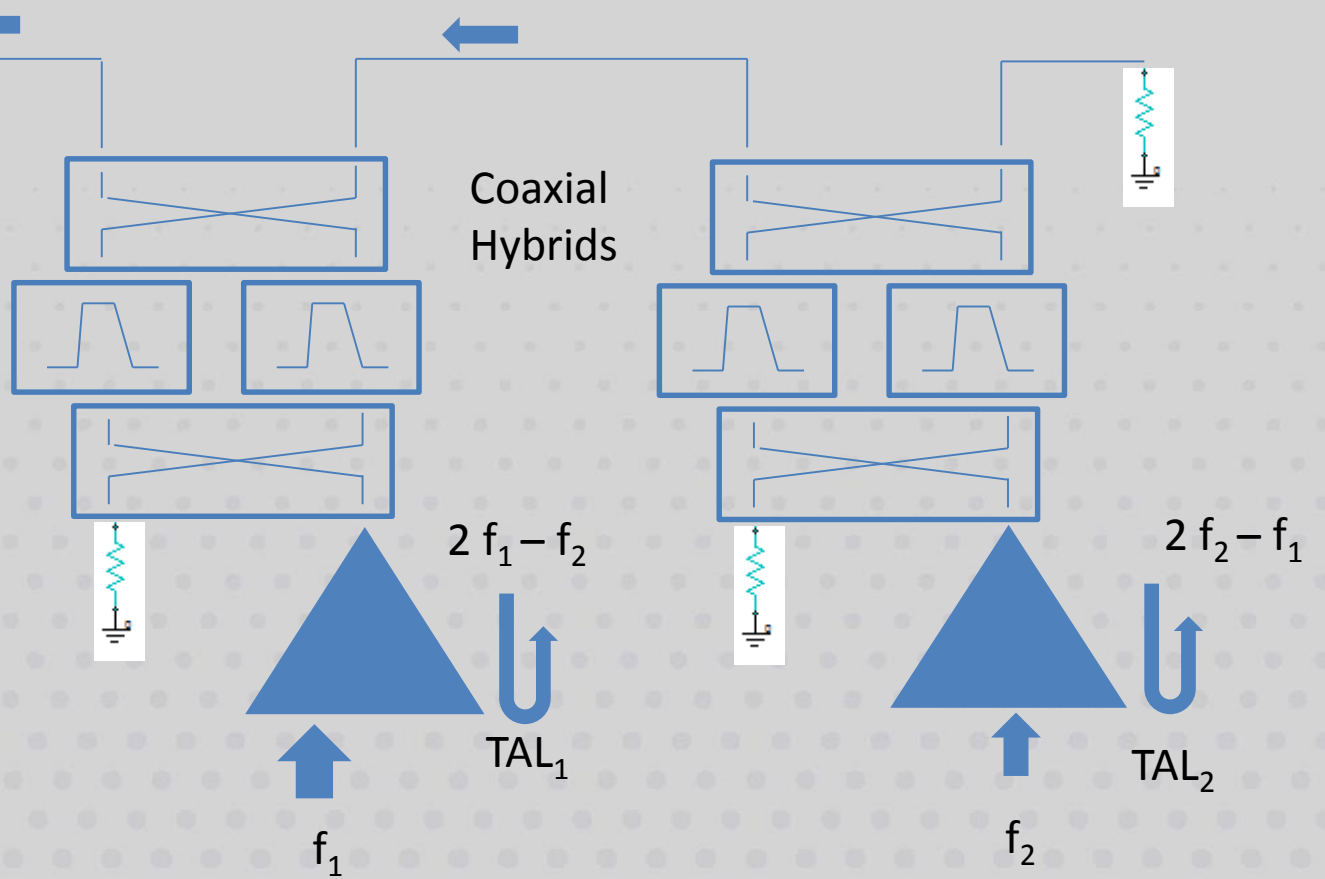Hybrids add 30 to 35 dB of IM suppression on top of filter rejection and TAL


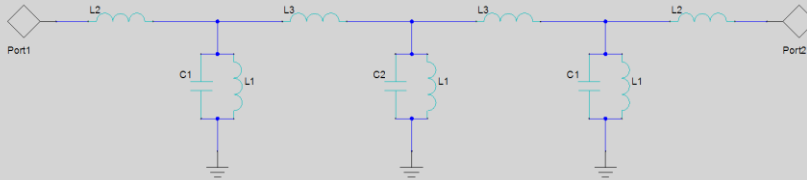
# Chebyshev Filters



Sequentially coupled from input to output



Lump element inductively coupled filter



Coupling routing diagram

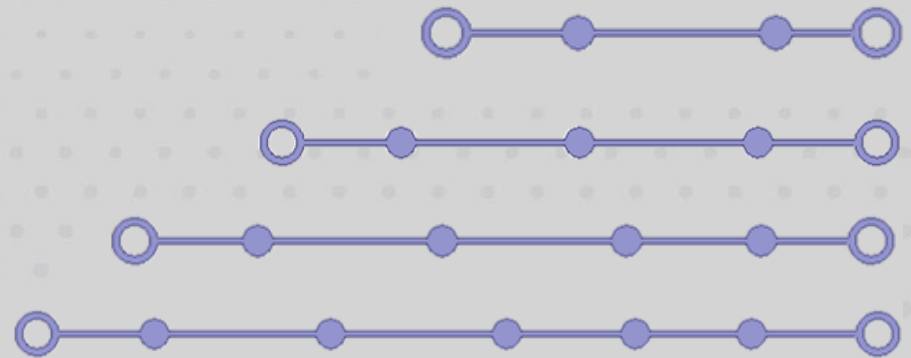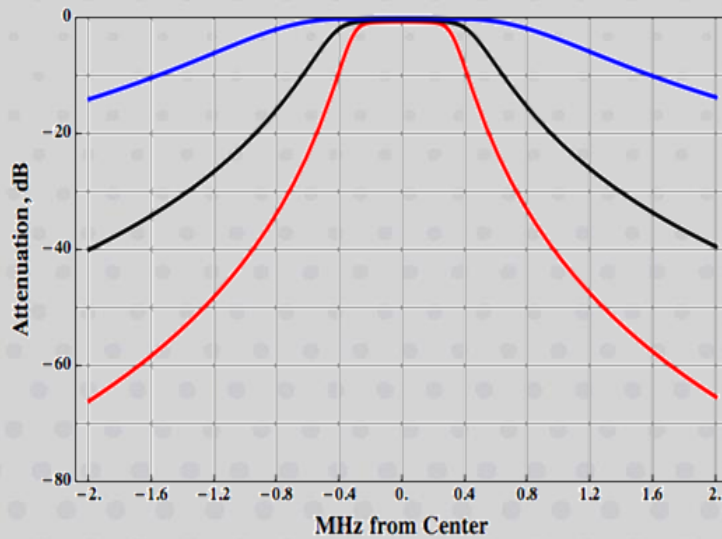

Two - Five Pole are used in FM Combining



# Chebyshev Filters - Channel Spacing and Efficiency

Minimum Channel Spacing  
to get -80 dB IM Suppression

# of poles	spacing in MHz	
	CIF	manifold
2	4.4	10.2
3	1.6	2.6
4	0.8	1.6
5	any	0.8


Efficiency vs. # of poles vs. Cavity size

# of poles	24" cavity	14" cavity	6" cavity
2	97.7%	96.6%	95.5%
3	96.6%	94.4%	91.6%
4	94.4%	92.2%	85.5%
5	92.2%	88.1%	77.6%

Efficiency  $\propto$  Insertion Loss  $\propto$  Cavity Size



# Combining Requirements

## 1.6 MHz Spacing Example

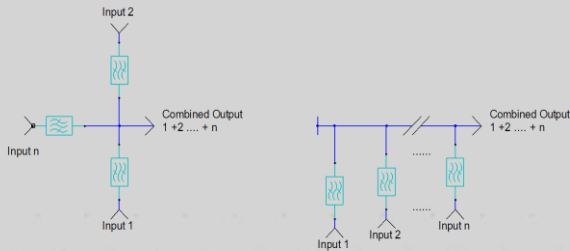

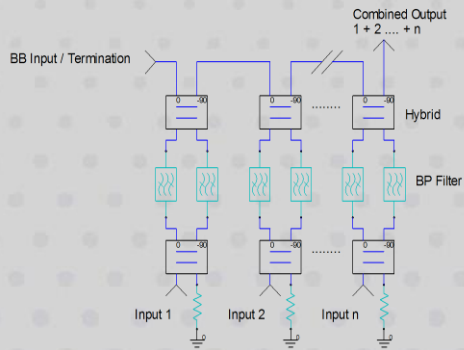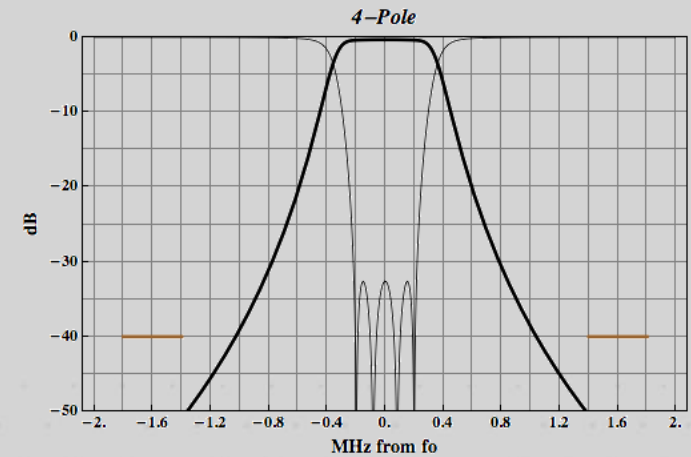
### Junction Combiner

- Isolation entirely dependent on filter
- ∴ 40 dB min filter rejection
- 4-pole required for 1.6 MHz spacing


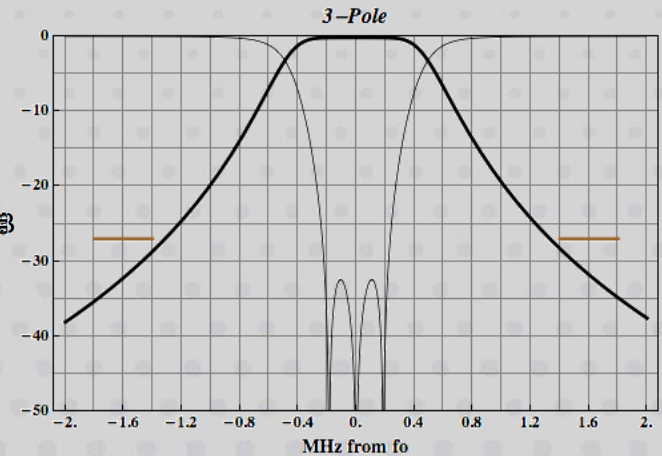
### Directional Combiner


- Hybrids provide directionality (isolation), ~ 30 dB
- ∴ 27-30 dB min filter rejection
- 3-pole required for 1.6 MHz spacing






# Cross Coupled Filters; Tri-Circuit


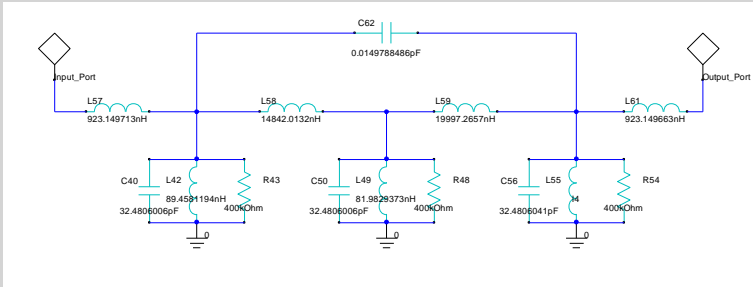
## Coupling Introduced between Non-Adjacent Resonators



Lump element inductively coupled filter

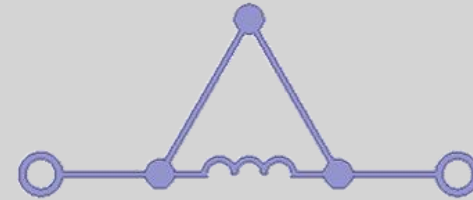


Coupling routing diagram

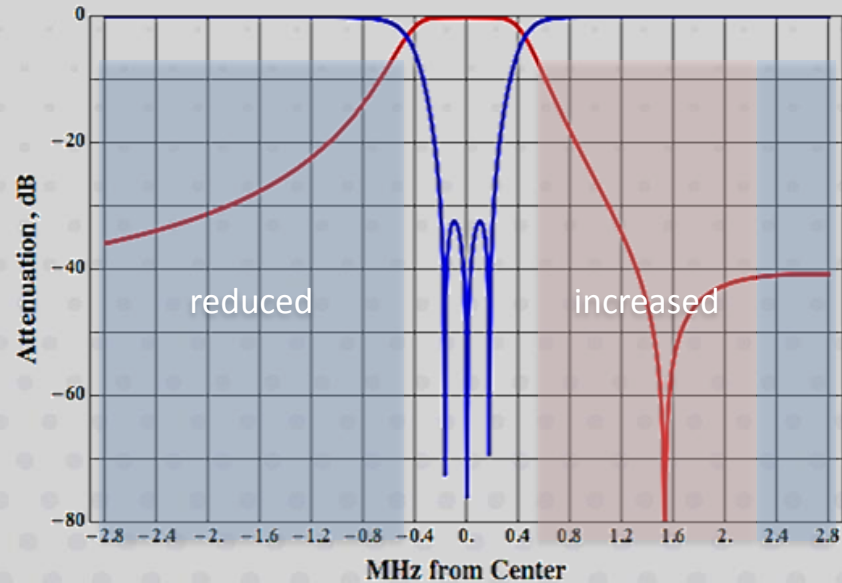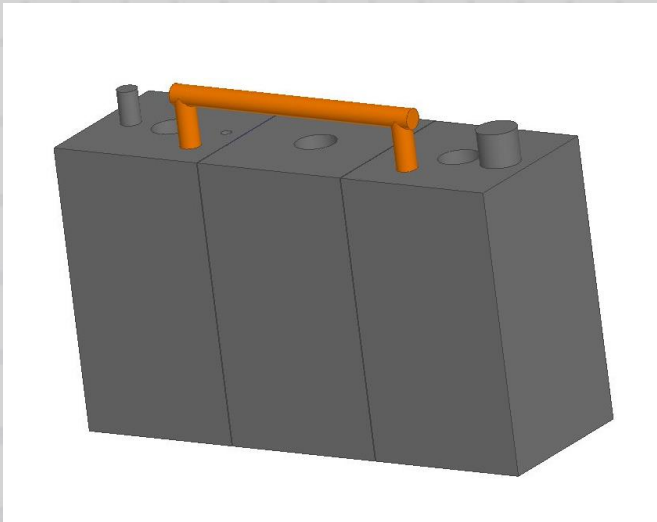


Allows for closer channel combining but no significant increase in IM suppression

# Cross Coupled Filters; Quad-Circuit

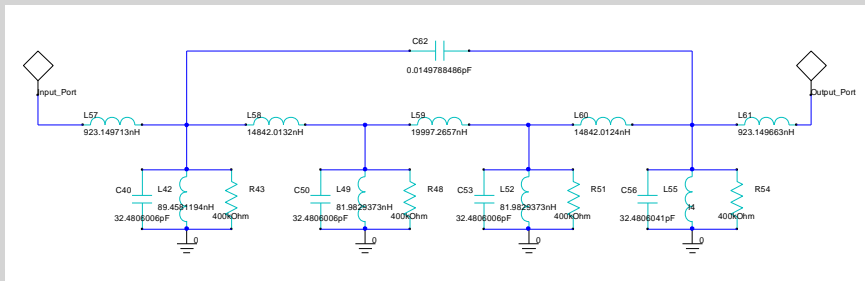
## Coupling Introduced between Non-Adjacent Resonators



Lump element inductively coupled filter


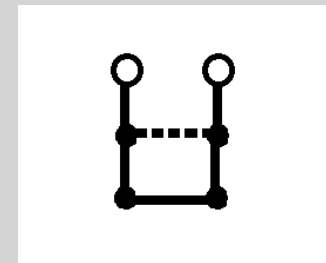


Coupling routing diagram

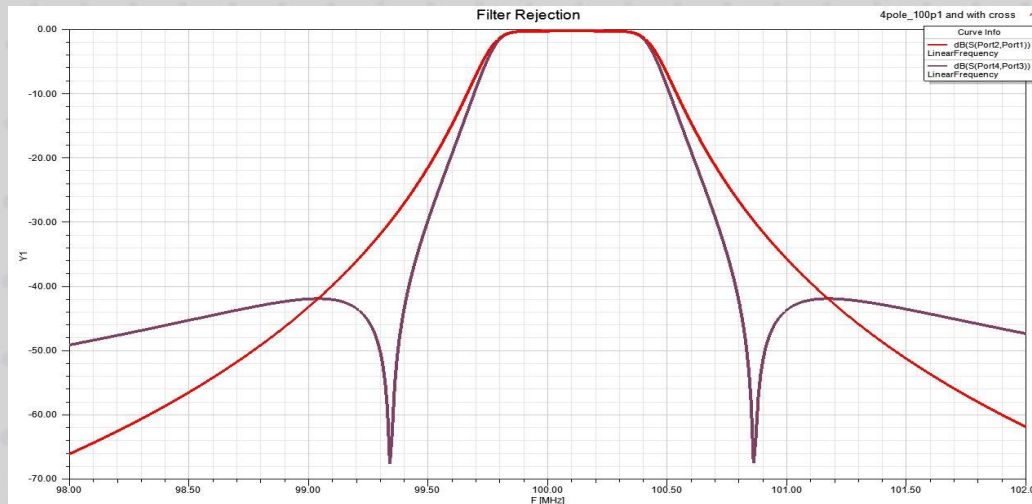


Allows 4 pole to be used for 800 kHz and greater spacing in manifold combiner
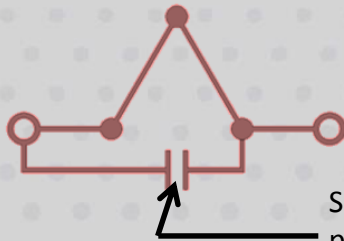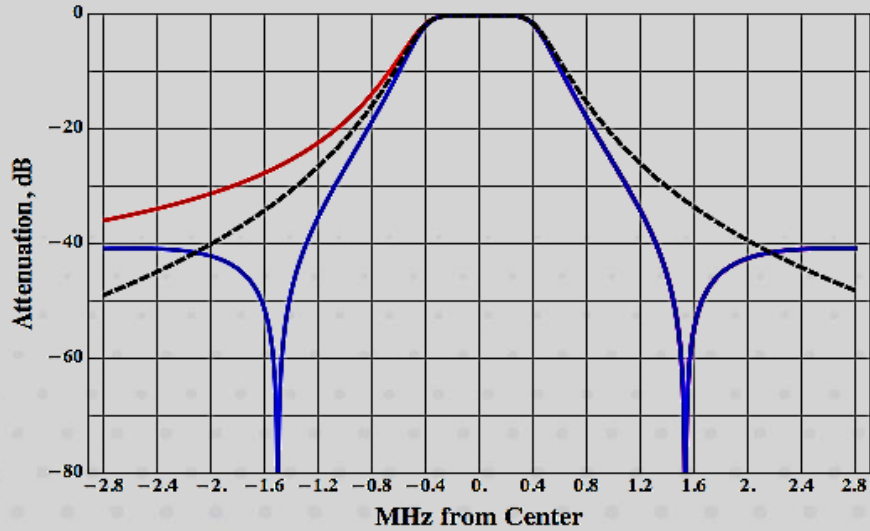
# *New* Cross Coupled Filter – Source to Resonator Three Coupling


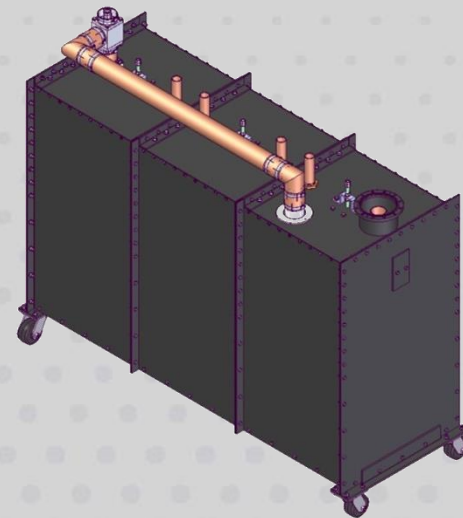
## Implemented with:

- Coaxial Tee at Input
- "Towel Rack" to Resonator Three
- Proper Coupling Structure in Resonator Three



Trusted for Decades. Ready for Tomorrow.



# **New** Cross Coupled Filter – Source to Resonator Three Coupling

Minimum Channel Spacing  
to get -80 dB IM Suppression

# of poles	spacing in MHz	
	CIF	manifold
2 cheb	4.4	10.2
3 cheb	1.6	2.6
3 w/ s-3 X	1.2*	1.6
4 cheb	0.8	1.6
4 w/ 1-4 X	any	0.8
5 cheb	any	0.8


\* 0.8 MHz if TAL is included

Cross coupled filters  
offer higher rejection  
without increased  
insertion loss

- Lower Loss
- Lower Group Delay
- Smaller Size


# New Source/Load Multi-Resonator Coupling

Solution for an Efficiency Problem

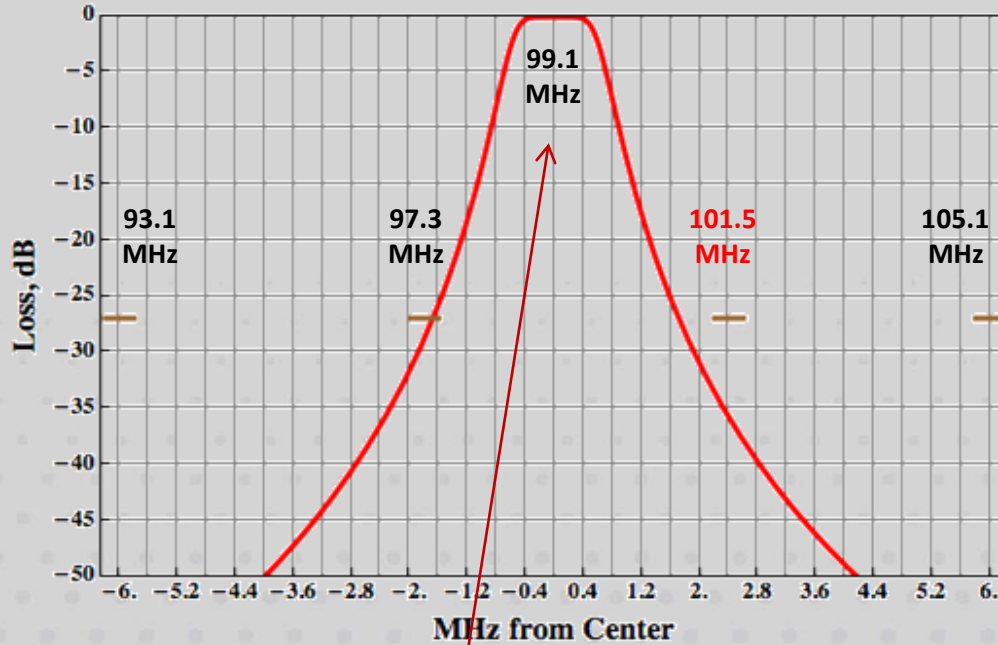

$n = 3$   
 $VSWR = 1.05$   
 $BW_r = 550\text{kHz}$   
 $Loss_{f_0} = .128\text{ dB}$

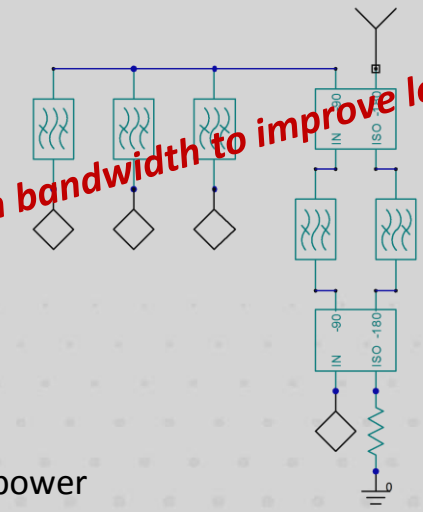
How far can I open bandwidth to improve loss?



- 99.1 MHz, high power
  - No Tx headroom
  - 3-pole filters to minimize loss
  - **< .1 dB loss required**
- 101.5 MHz may come in later

# New Source/Load Multi-Resonator Coupling

Loss vs Bandwidth


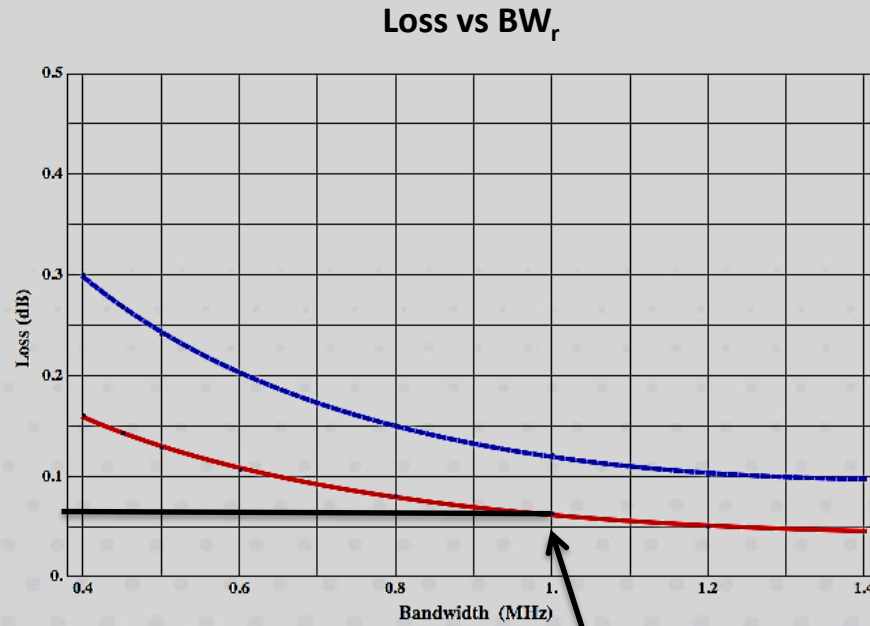


Need  $\approx 1$  MHz  $BW_r$

- 24" Cavity
- 3-pole red
- 4-pole blue

# New Source/Load Multi-Resonator Coupling

*SOLUTION to an Efficiency Problem*

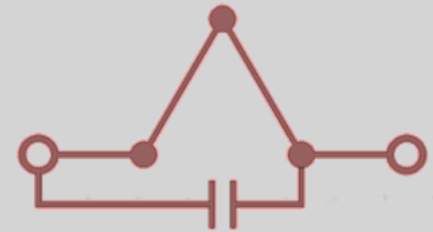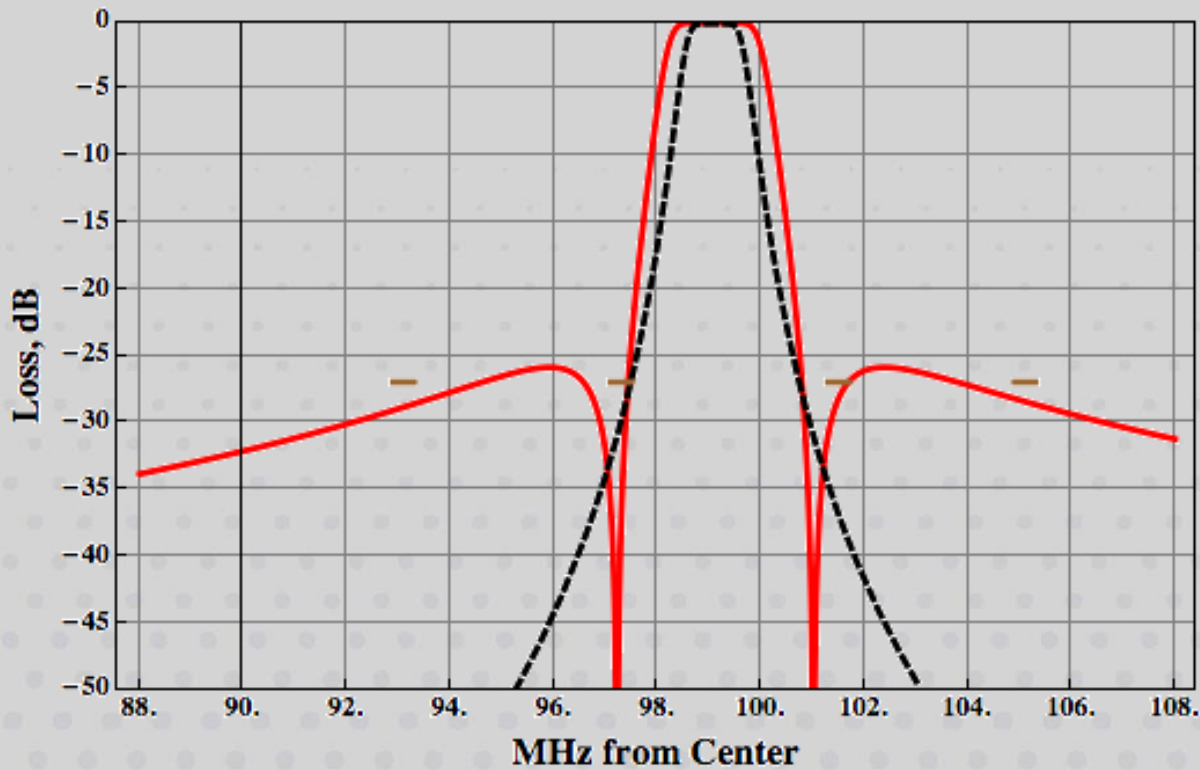

**n = 3**  
**VSWR = 1.12**  
**BW<sub>r</sub> = 1150kHz**  
**Loss<sub>f0</sub> = .06 dB**



Trusted for Decades. Ready for Tomorrow.


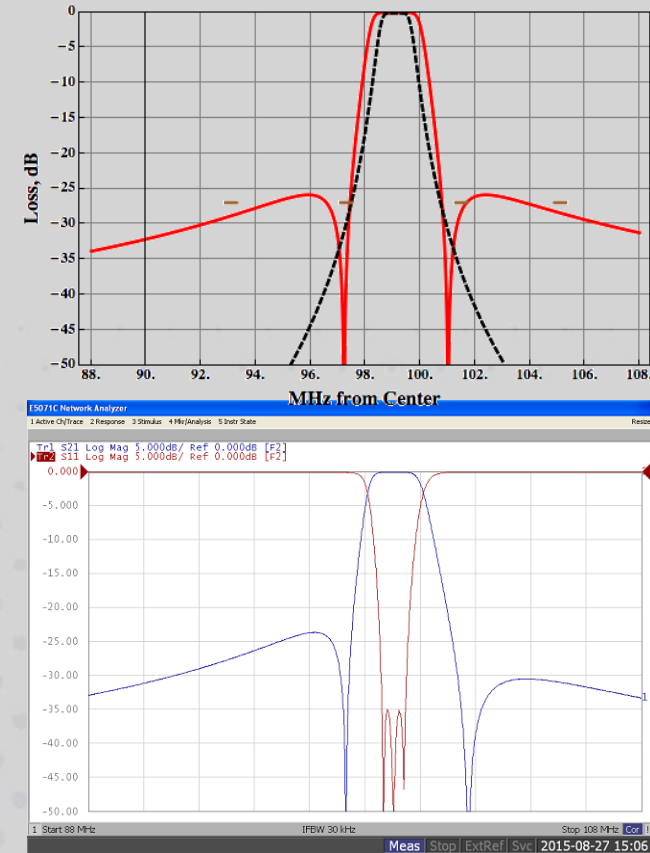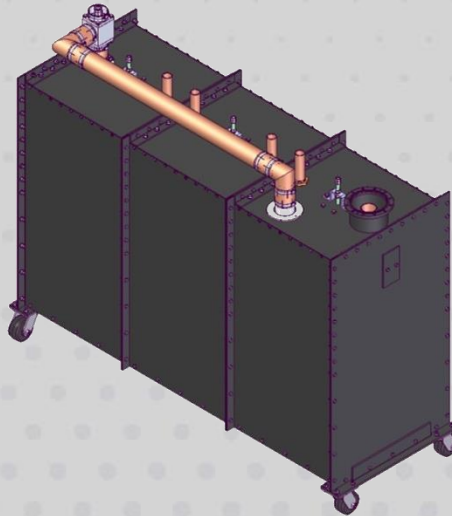
# New Source/Load Multi-Resonator Coupling

SOLUTION to an Efficiency Problem


- Source to three used on a 3-pole filter
  - Provide transmission zeros
  - Increase efficiency with wider bandwidth
- Filter loss:
  - < .16 dB w/o X-coupling
  - < .06 dB with X-coupling



Trusted for Decades. Ready for Tomorrow.




# Efficiency Manifold or Directional

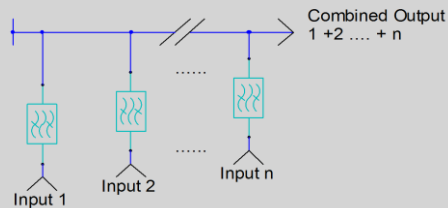
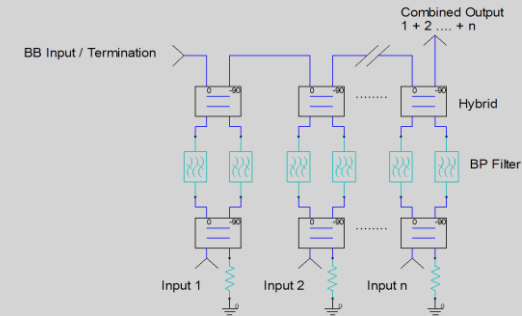
## Manifold


- More efficient
- All channels same VSWR
- All channels same loss
- Mainline offers higher voltage safety margin
- Compact, light and simple
- Easy to assemble
- Easy to test
- Easily maintainable
- Lower cost (by 60%)
- Simple module design and installation
- Non – Expandable
- Power Limited
- Need to be properly phased with tube transmitters



## Directional

- Less efficient
- VSWR degrades with distance
- Loss degrades with distance
- Hybrids limit voltage safety margin
- Large, heavy and complex
- Difficult to assemble
- Difficult to test
- Difficult to maintain
- Higher cost
- Part intense module design
- Expandable
- Doubles Filter Power
- Works well with tube transmitters

# Manifold Combiner

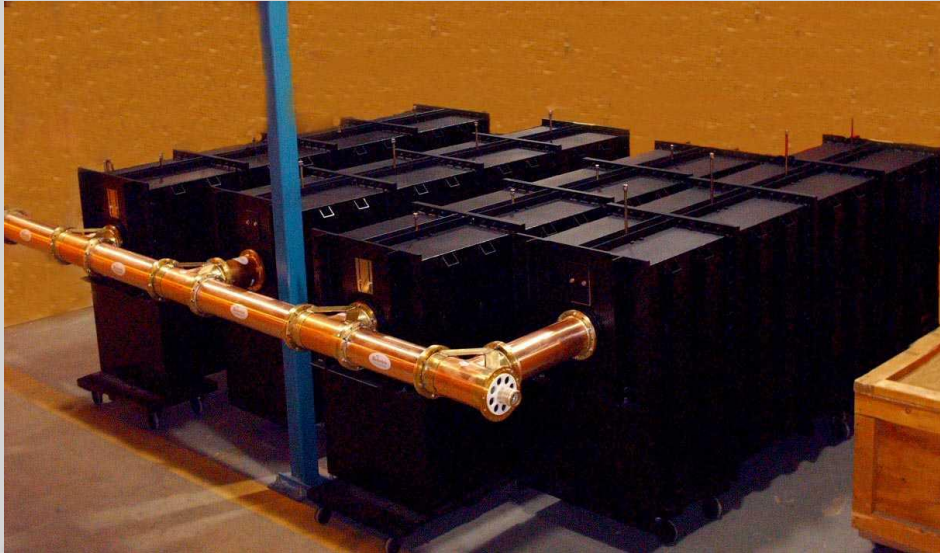

## 4-Channel Manifold

- Band pass filter, tee, delay line
- Tees spaced  $\approx n \lambda/2$
- Traditionally limited to 6 channels or less due to difficulty of cut and try design method


Trusted for Decades. Ready for Tomorrow.

# Manifold Combiner

Modern CAD tools make manifold design more predictable


Site requires 10 channel manifold

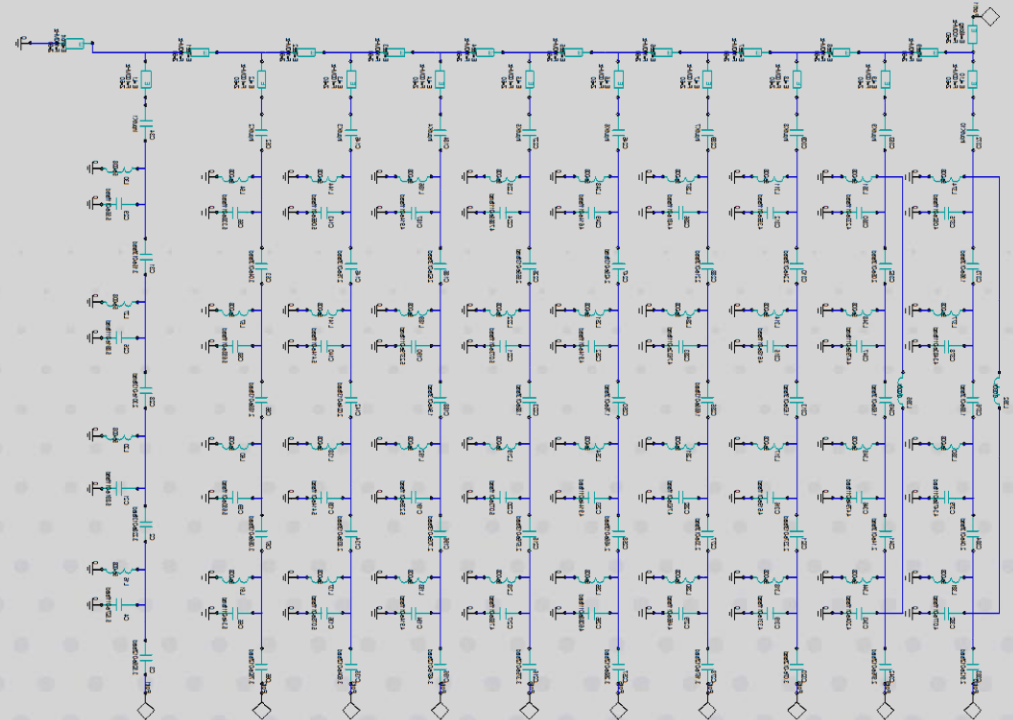Decided to design and build using 6" cavity filters



# Manifold Combiner Lumped Element Model

## Optimized Results

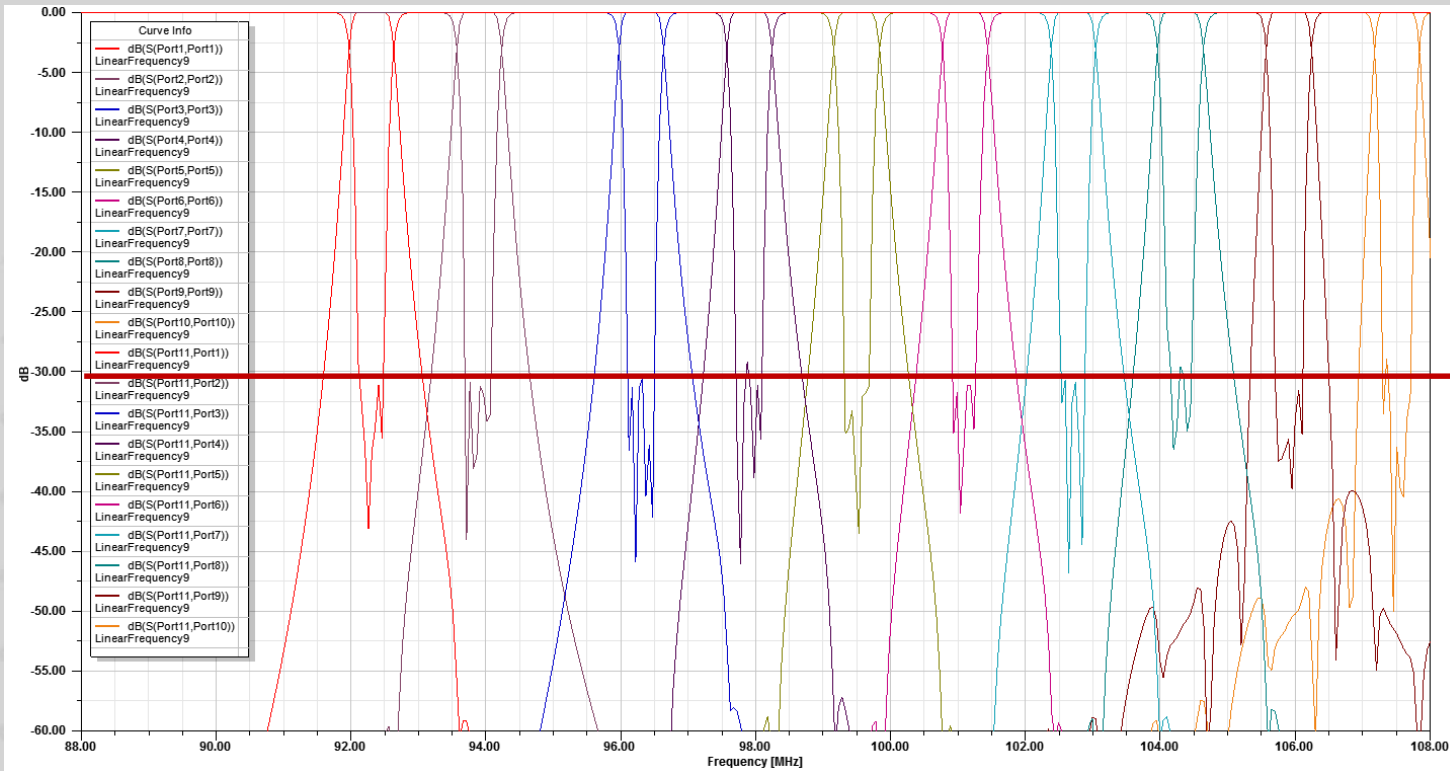

Trusted for Decades. Ready for Tomorrow.



# 10 Channel LPFM Combiner *In line configuration*




Trusted for Decades. Ready for Tomorrow.



# 10 Channel LPFM Combiner
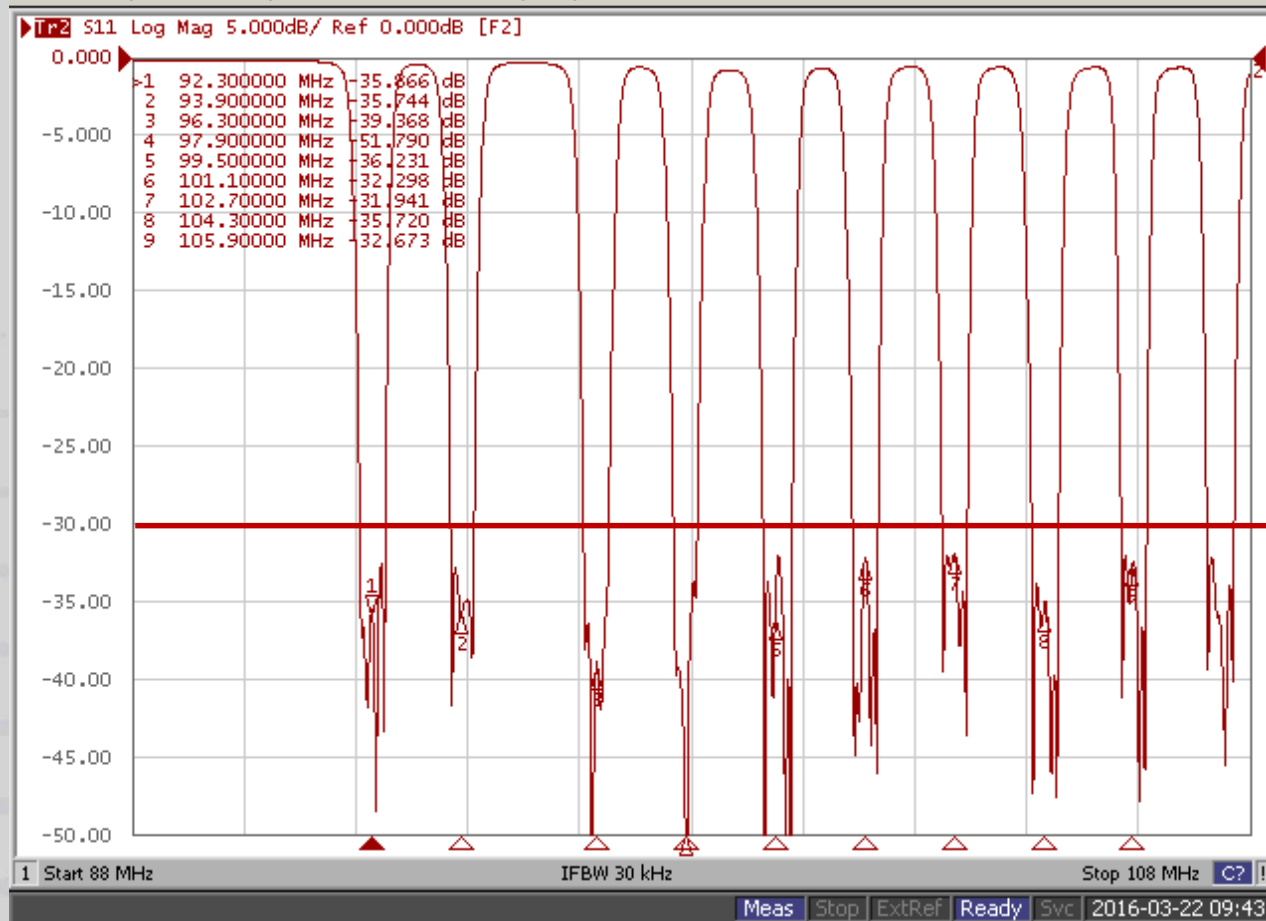
## *Actual Data, Post Optimization Return Loss*




> -30 dB

Trusted for Decades. Ready for Tomorrow.

# 10 Channel LPFM Combiner

## *Actual Data, Post Optimization*

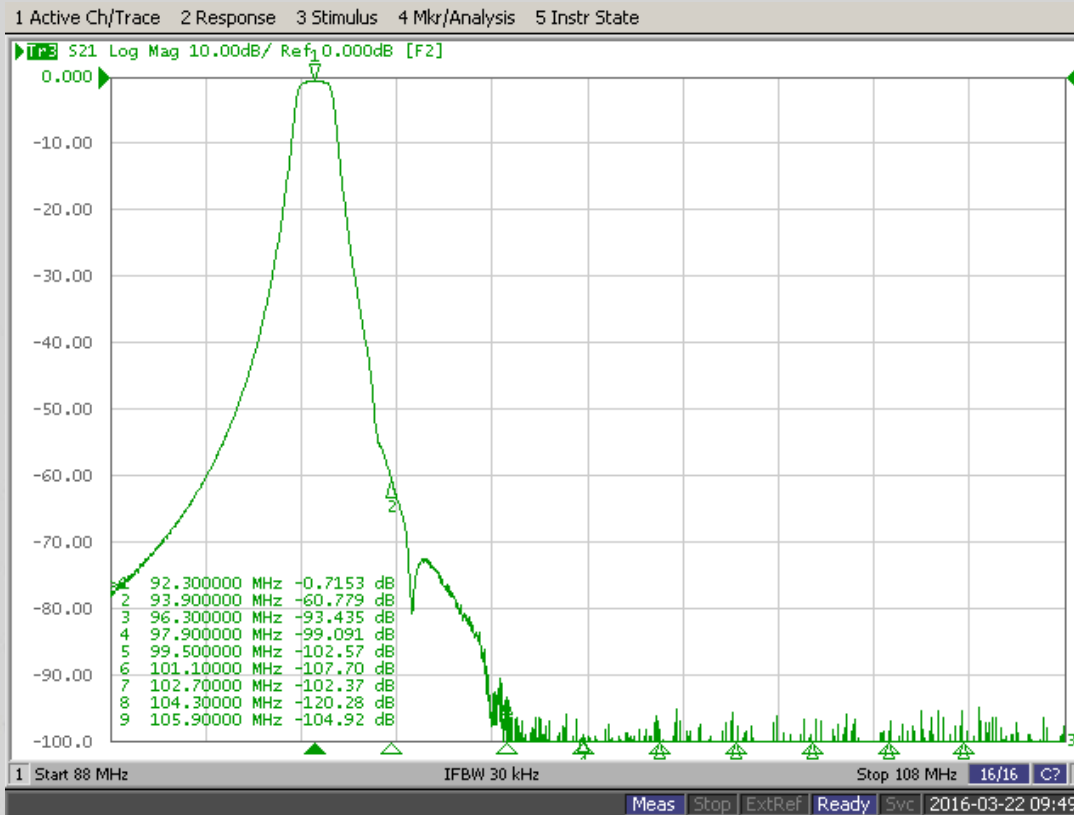


<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB

Trusted for Decades. Ready for Tomorrow.

# 10 Channel LPFM Combiner

## *Actual Data, Post Optimization*

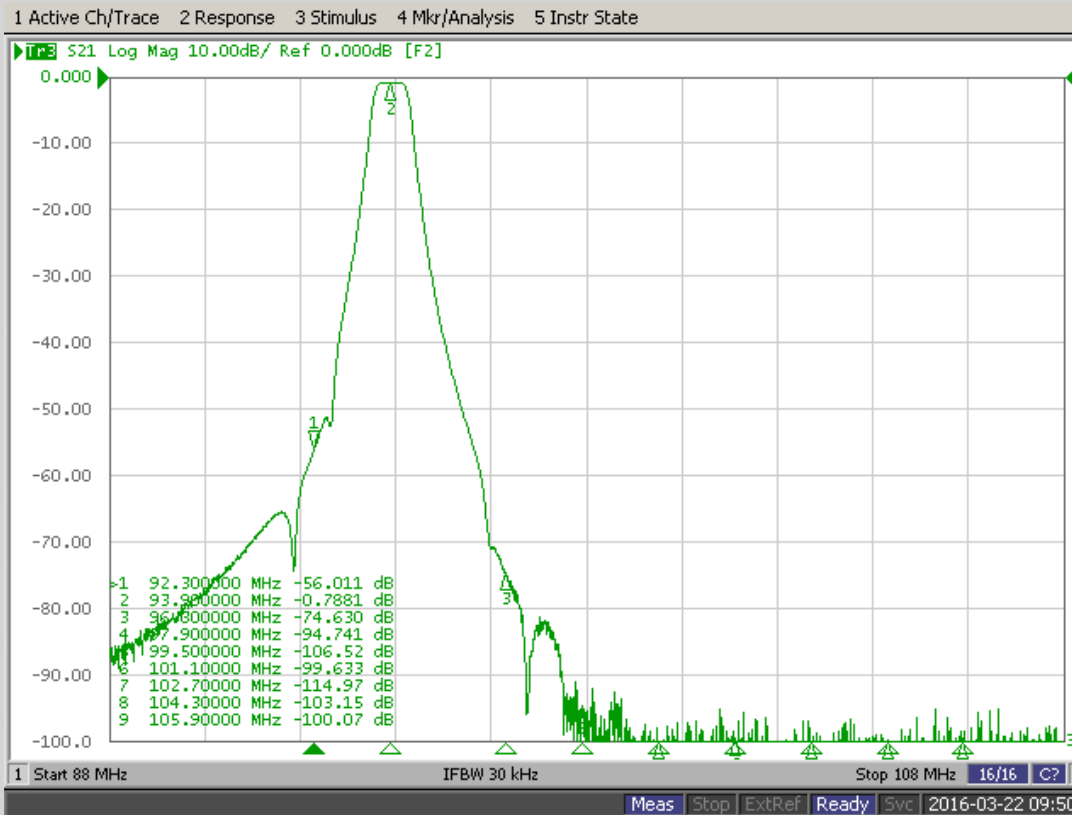

**Combiner**

**Channel**

**Loss**

92.3MHz


.72dB

93.9MHz

.79dB

**Trusted for Decades. Ready for Tomorrow.**
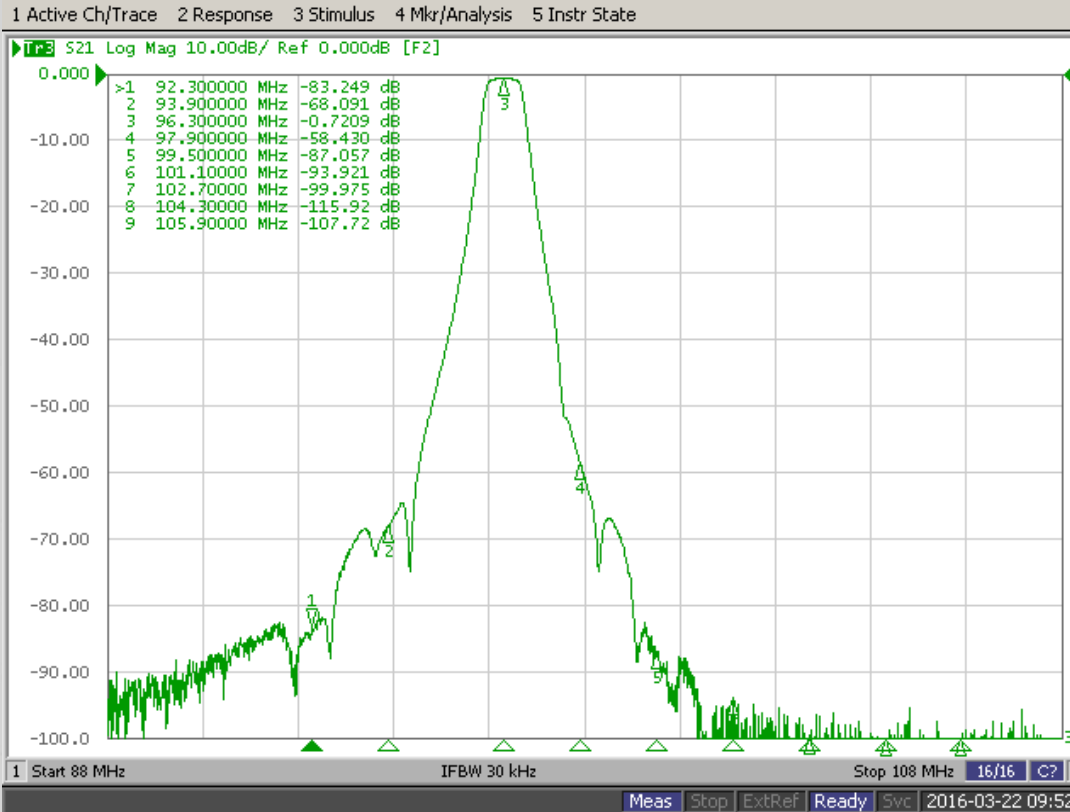
# 10 Channel LPFM Combiner Actual Data, Post Optimization




<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB

Trusted for Decades. Ready for Tomorrow.


# 10 Channel LPFM Combiner

## Actual Data, Post Optimization

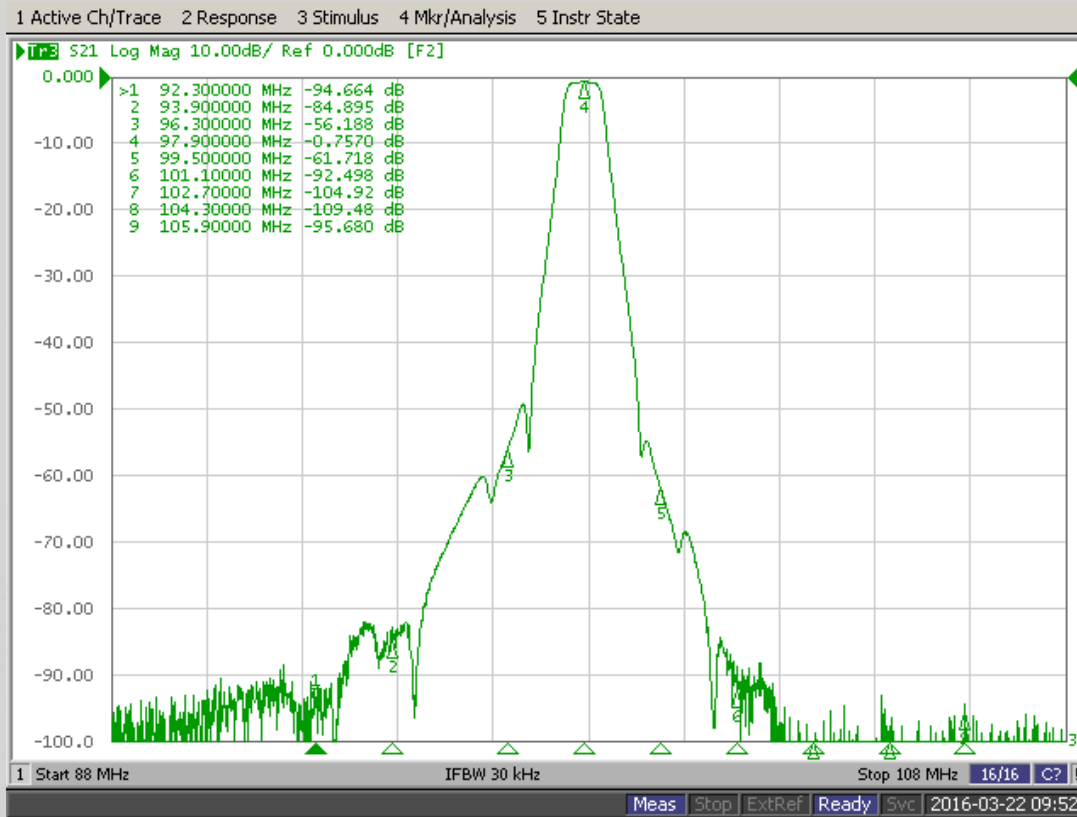

<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB

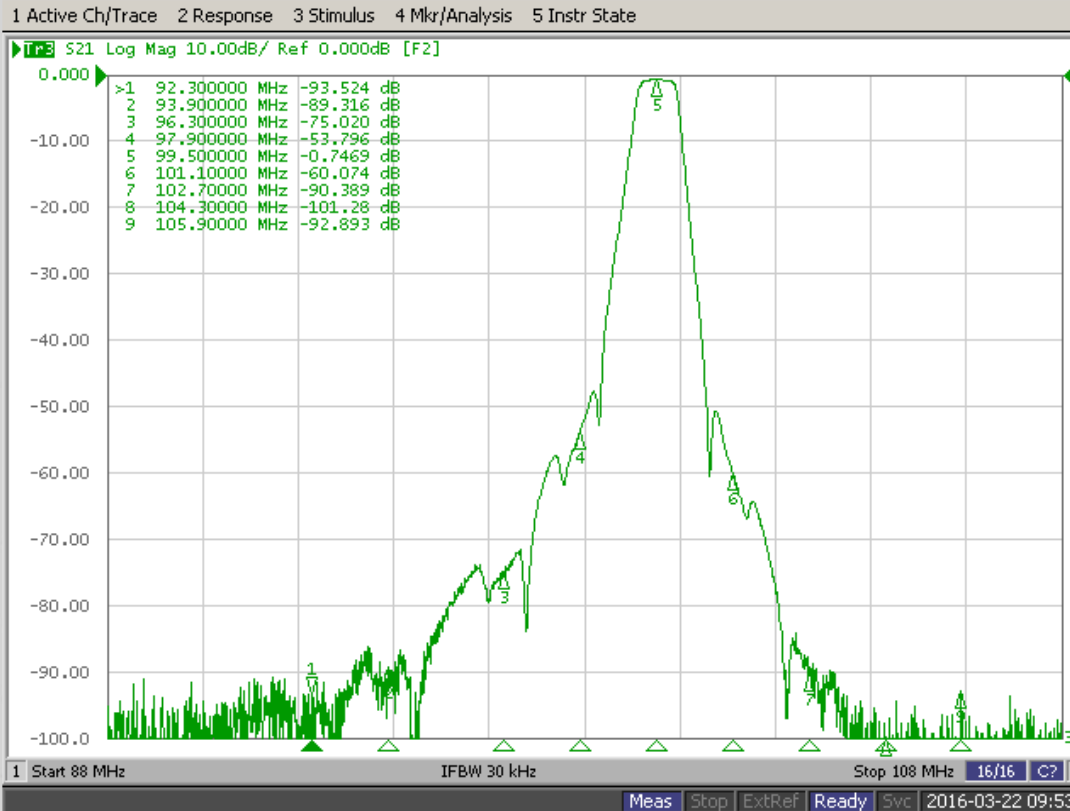
# 10 Channel LPFM Combiner Actual Data, Post Optimization



<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB
99.5MHz	.75dB

Trusted for Decades. Ready for Tomorrow.
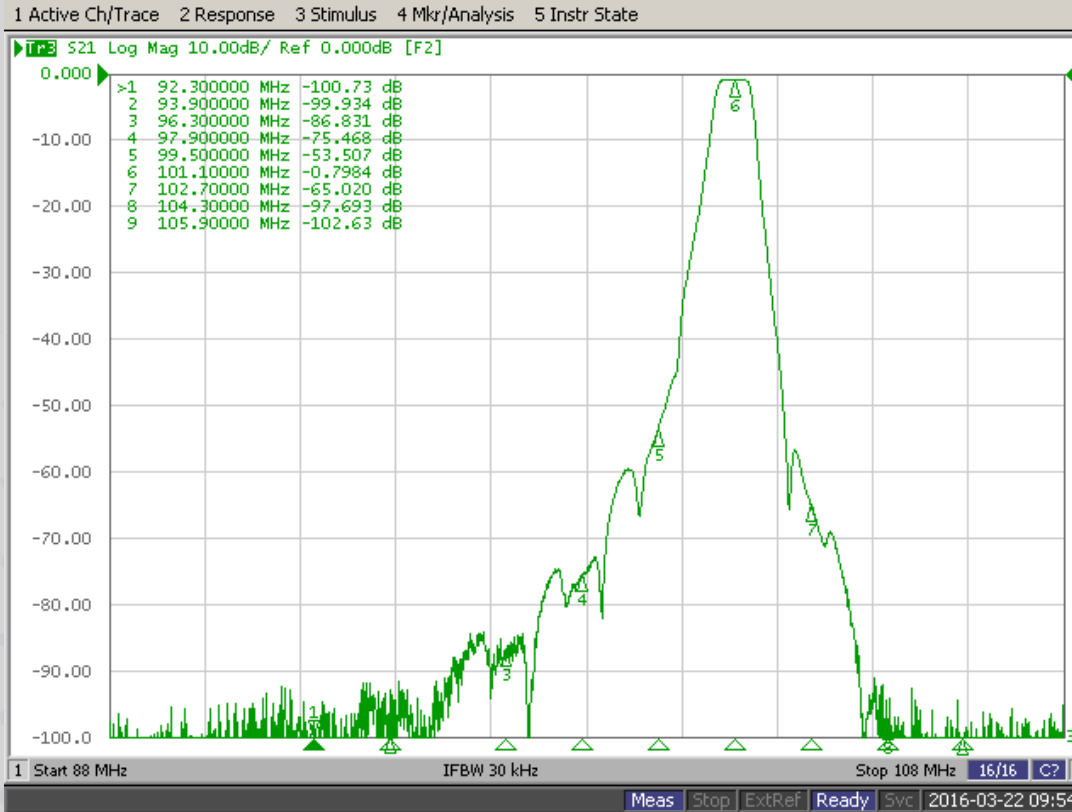
# 10 Channel LPFM Combiner Actual Data, Post Optimization



## Combiner


<u>Channel</u>	<u>Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB
99.5MHz	.75dB
101.1MHz	.80dB

Trusted for Decades. Ready for Tomorrow.



# 10 Channel LPFM Combiner


## Actual Data, Post Optimization

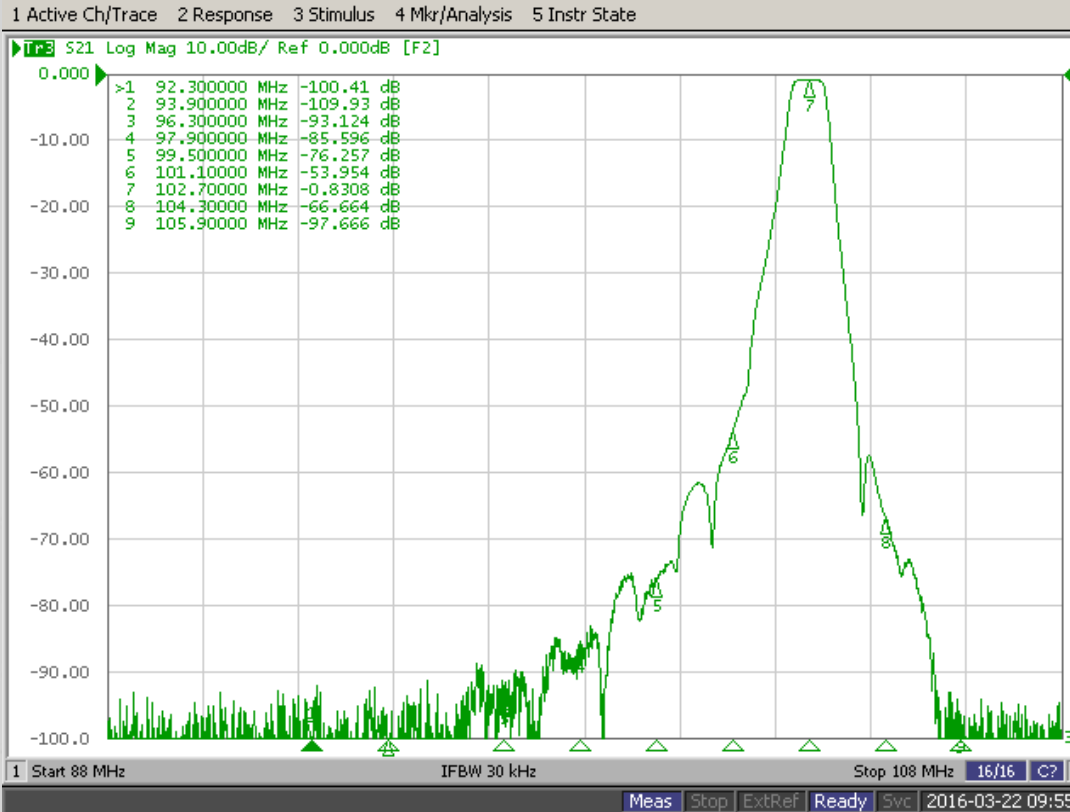

<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB
99.5MHz	.75dB
101.1MHz	.80dB
102.7MHz	.83dB
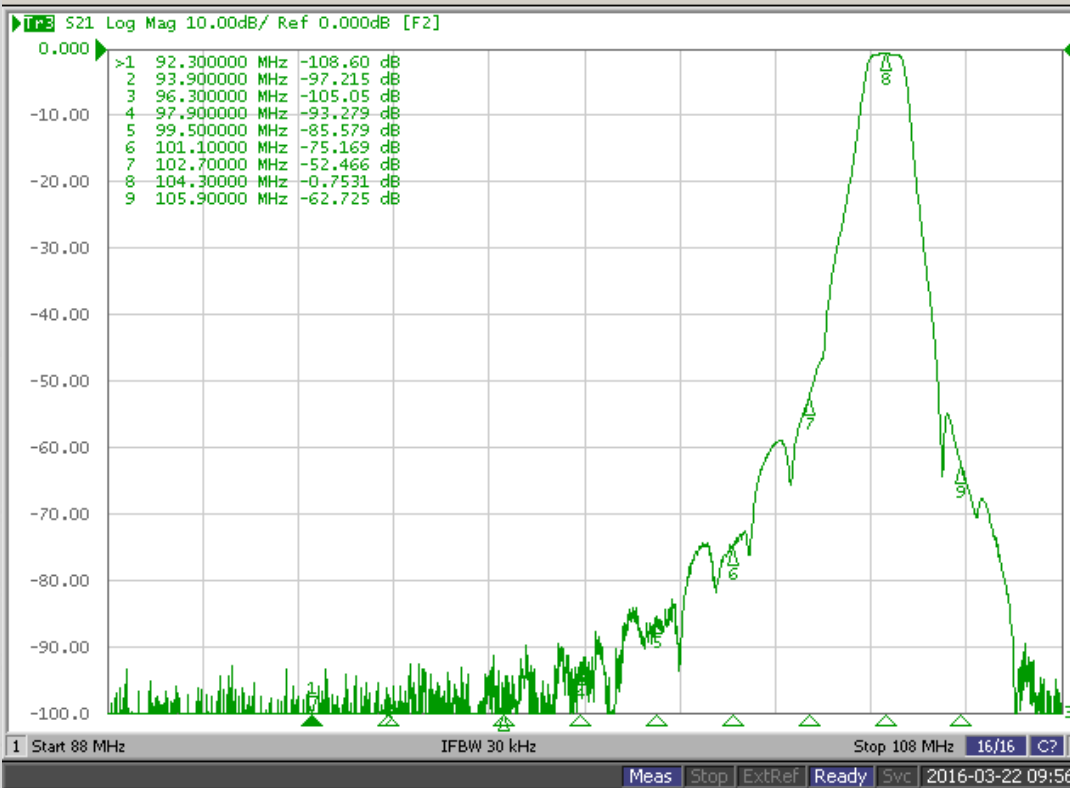
# 10 Channel LPFM Combiner Actual Data, Post Optimization

1 Active Ch/Trace 2 Response 3 Stimulus 4 Mkr/Analysis 5 Instr State



**Combiner**


<u>Channel</u>	<u>Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB
99.5MHz	.75dB
101.1MHz	.80dB
102.7MHz	.83dB
104.3MHz	.75dB

Trusted for Decades. Ready for Tomorrow.

# 10 Channel LPFM Combiner
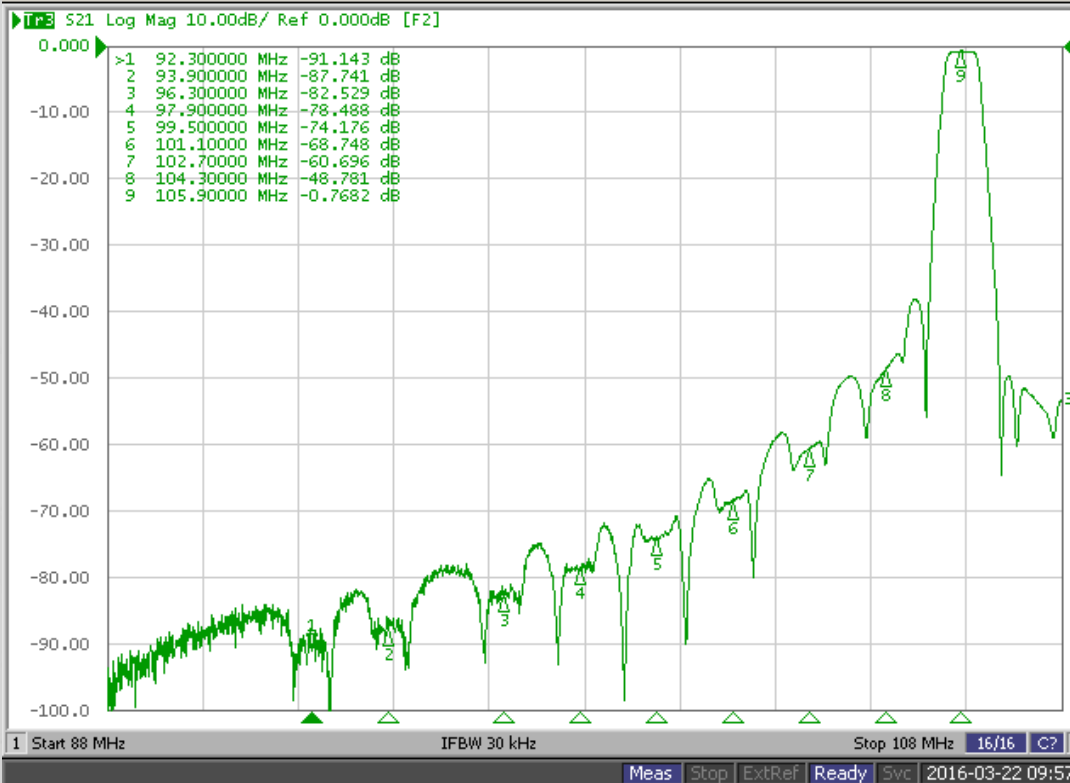
## Actual Data, Post Optimization

1 Active Ch/Trace 2 Response 3 Stimulus 4 Mkr/Analysis 5 Instr State




<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB
99.5MHz	.75dB
101.1MHz	.80dB
102.7MHz	.83dB
104.3MHz	.75dB
105.9MHz	.77dB

Trusted for Decades. Ready for Tomorrow.

# 10 Channel LPFM Combiner

## Actual Data, Post Optimization

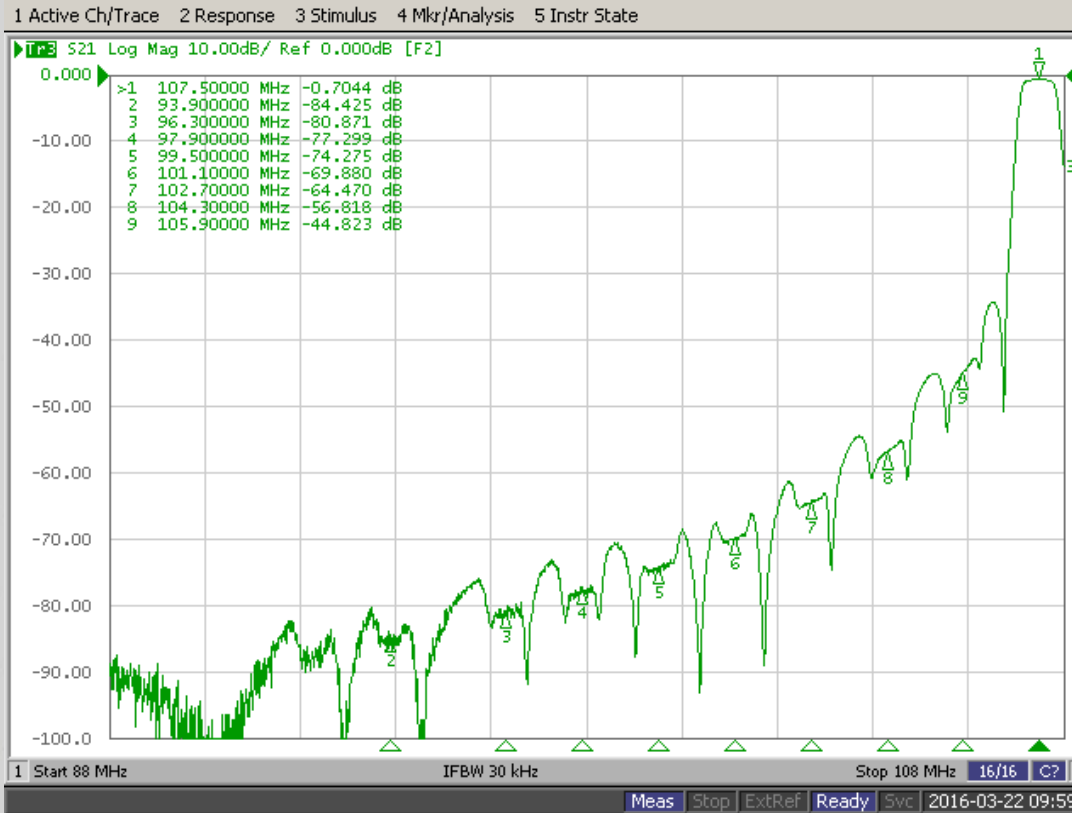


<u>Channel</u>	<u>Combiner Loss</u>
92.3MHz	.72dB
93.9MHz	.79dB
96.3MHz	.72dB
97.9MHz	.76dB
99.5MHz	.75dB
101.1MHz	.80dB
102.7MHz	.83dB
104.3MHz	.75dB
105.9MHz	.77dB
107.5MHz	.70dB

Trusted for Decades. Ready for Tomorrow.

# 10 Channel LPFM Combiner *Design/Optimization Time*
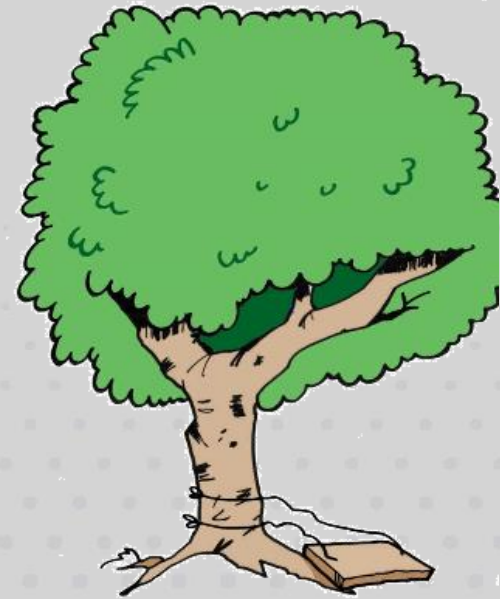
## Actual Duration Times:

- Lumped element design in ANSYS – 2 days
- Mechanical design – 1 day
- Manufacturing – 10 days
- Individual filter tuning – 0.5 days
- 10 channel manifold assembly/test – 0.5 day



AS DESIGNED BY  
ENGINEERING

# Manifold Combiner Benefits

- Better impedance for transmitters at ALL channels
- Higher efficiency for ALL broadcasters
- Lower initial cost
- Lower operating cost
- Design/component simplicity
- Reduced size

Cross coupled filters  
allow lower order filters  
in manifold combiners!

## Specification

## Manifold

## CIF (# of modules from output)

VSWR

< 1.06:1

< 1.1:1 (1<sup>st</sup>, takes a beating for others )  
< 1.16:1 ( 10<sup>th</sup>, pays dearly for position)

Loss,  $f_0$

< .35 dB

< .35 dB (1<sup>st</sup> and keeping quite about it)  
< .95 dB (10<sup>th</sup> no beer money left)



Trusted for Decades. Ready for Tomorrow.



THANKS FOR YOUR TIME!  
ANY QUESTIONS?



Dielectric<sup>®</sup>

Dielectric.com  @Dielectric\_LLC

Trusted for Decades. Ready for Tomorrow.